
# Information Technology for Digital Humanities Lecture 6


Mario Verdicchio
Università degli Studi di Bergamo
Academic Year 2024-2025

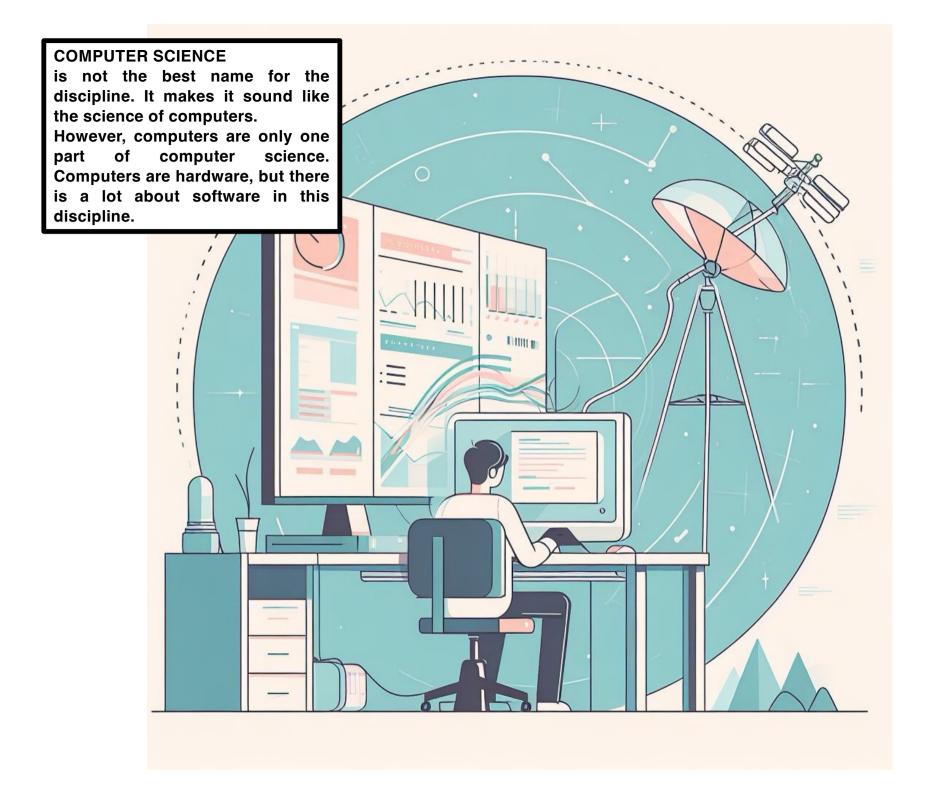
## Lecture 6 (October 9 2024)


- Computer science subfields
- Logic gates






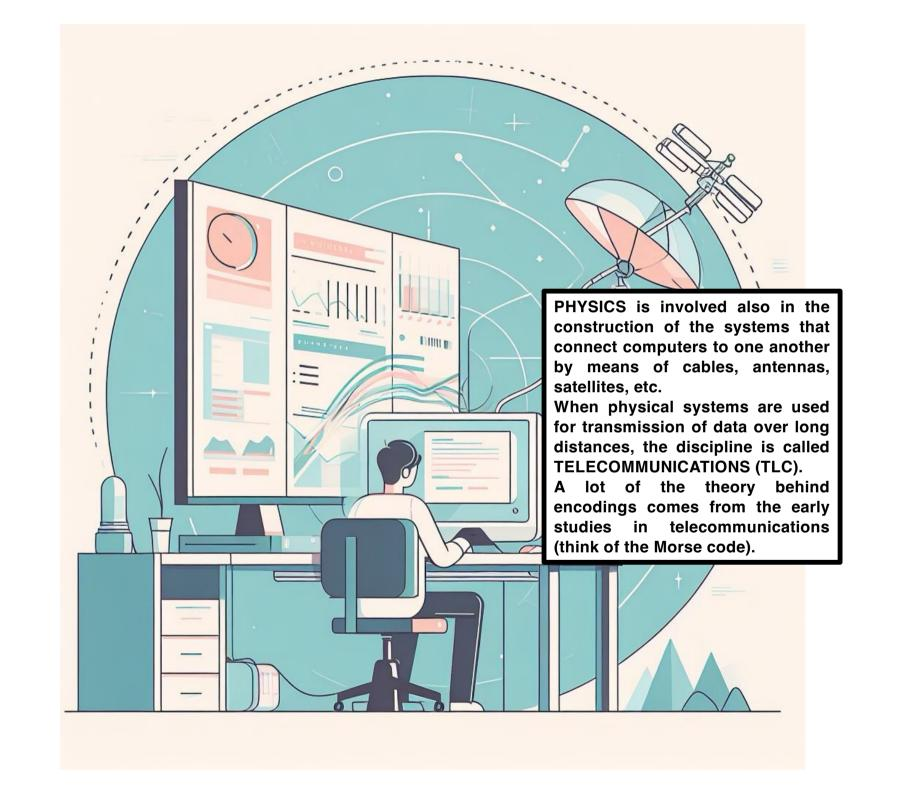

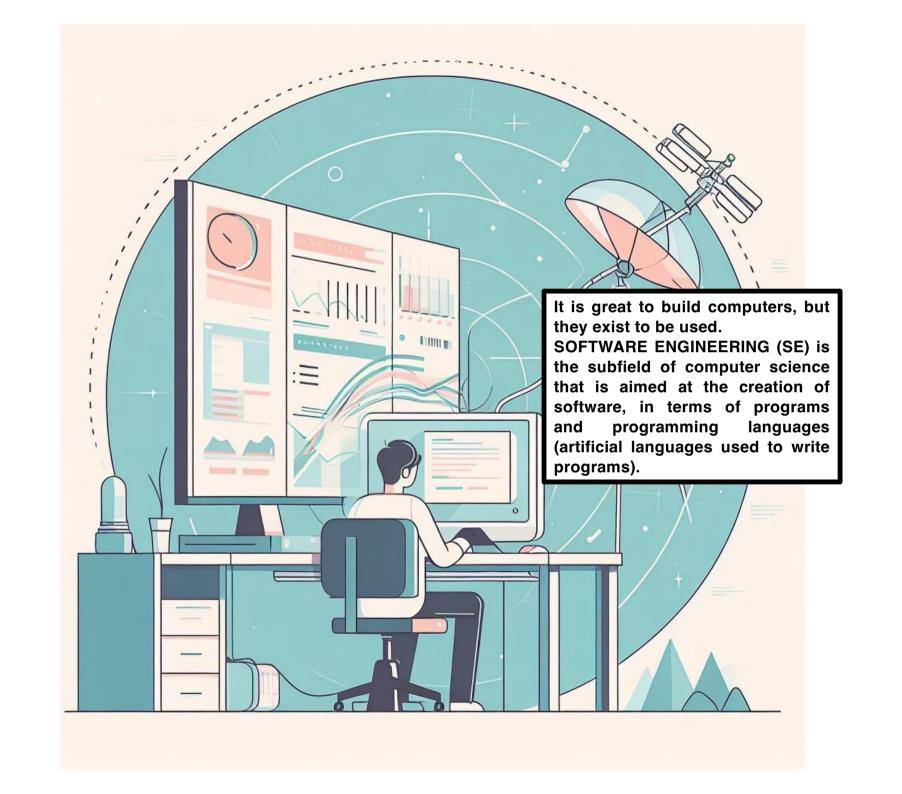

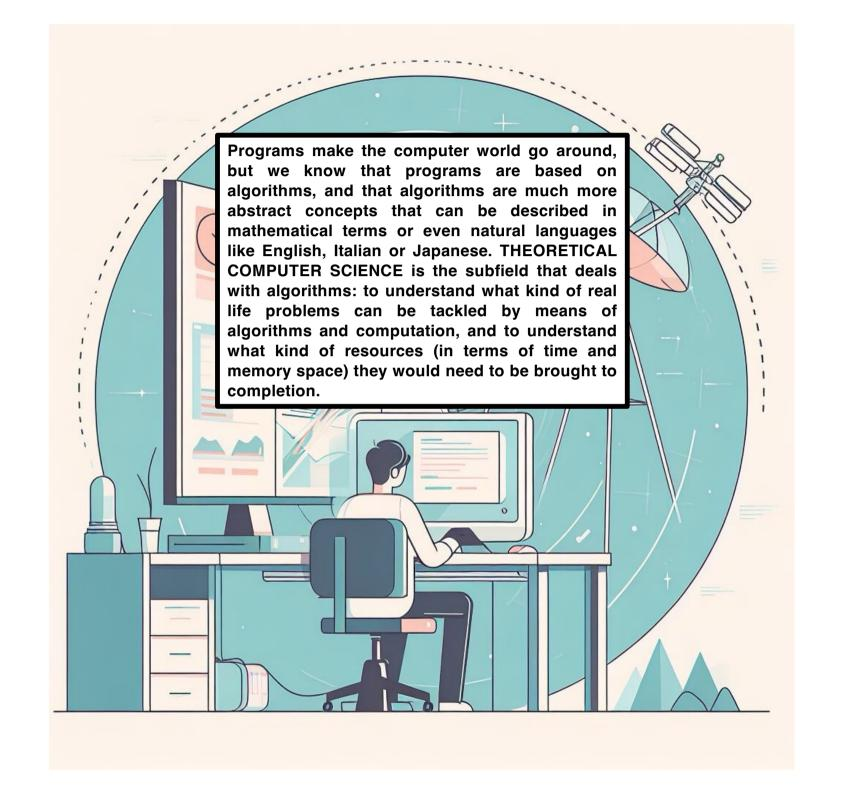

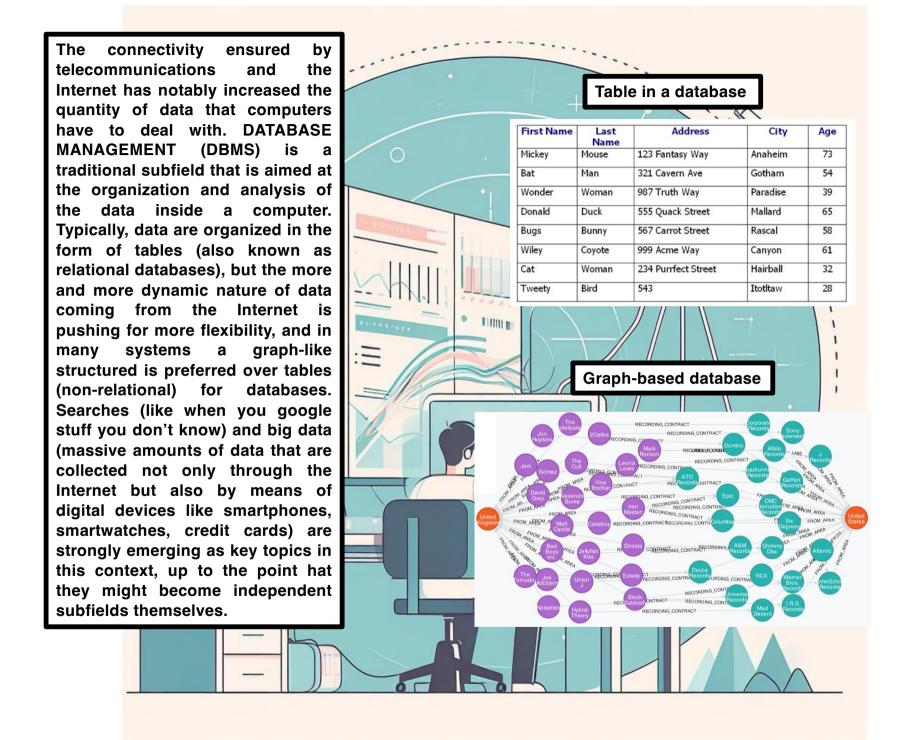




Finally, the hottest subfield of the moment: ARTIFICIAL INTELLIGENCE (AI). In its traditional form (it was born in the 1950s), Al was about "automated reasoning", that is, trying to capture in computational form the rules of logic that sustain human reasoning, to make computers do the reasoning. After decades of minor successes and major failures, another form of AI emerged, called "machine learning" (ML), which has a radically different approach: no more formal logical reasoning, but statistical analysis of great quantities of data, in search for correlations and recurrent patterns. ML is considered a major success because it just works, mainly thanks to the abundant quantities of data available on the Internet, which ML-programmed computers can analyse. The most successful applications are image analysis and classification (e.g. in the medical field to detect cancer from x-ray images), or text generation (e.g. ChatGPT) and image generation (e.g. Midjourney, DALL-E).

to a parabolic antenna."

This background image itself is the output of DALL-E, to which this input was given: "image in neat minimal graphical style with pastel colors depicting a person working in front of a desktop computer with a big screen showing the interface of a very complex word processing software, while the computer is connected to a cable that goes outside the room, connected

Tilliti no

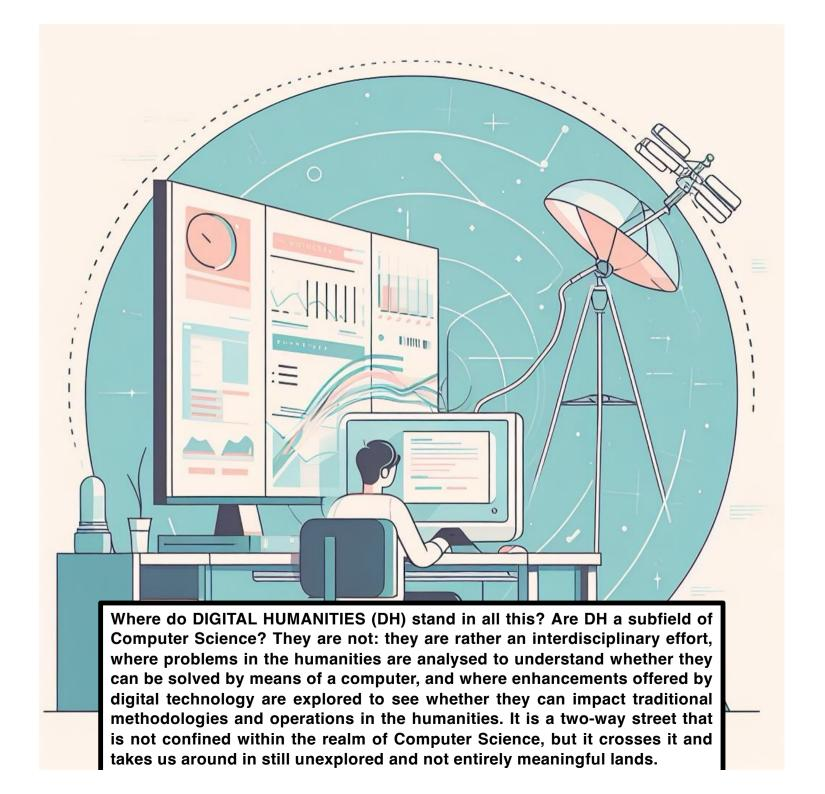


To understand how human choice maps onto parts of an electronic circuit, we must take a dive into the basic electronic components that constitute a computer hardware.

This technology dates back to the 1950s, when american scientists Bardeen, Brattain and Shockley invented the transistor, a small device based on a special property of semiconductive materials.

Semiconductive materials are particular: at rest, they do not allow electricity to flow, but if electrically stimulated they become conductive.

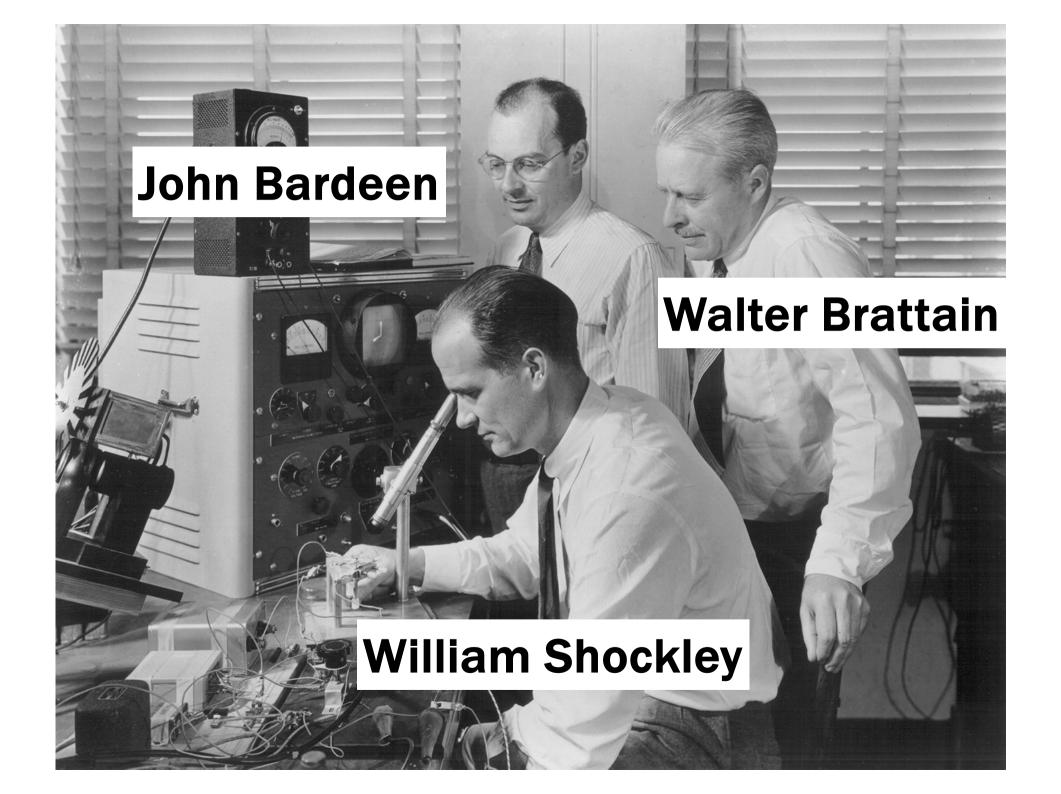
Hence, transistors are a special kind of switches: very small and electronic, that is, not mechanical but controlled by means of electricity.




#### a transistor from the 1950s

#### how it works



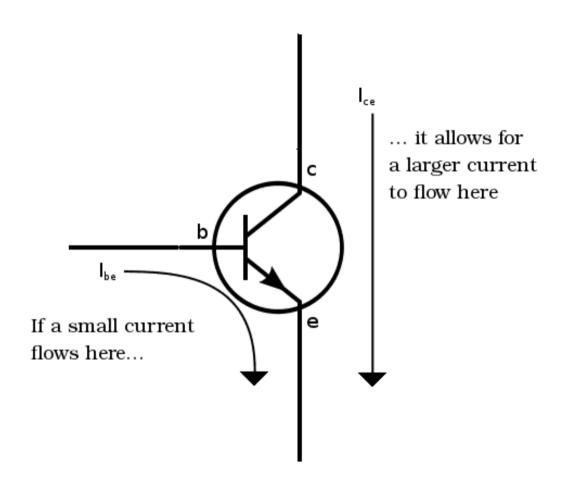
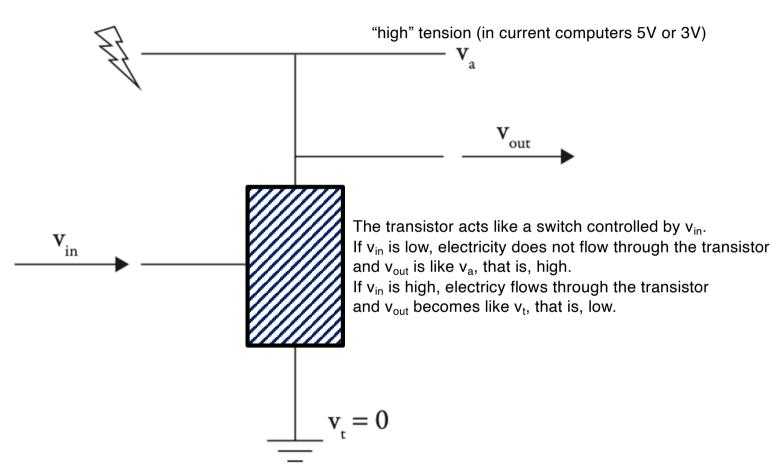
#### A more abstract description of a transistor



Ground: no tension here. Electricity flows from points of high tension to points of low tension.


### The fundamental encoding inside a computer



 $v_a$  ----- 1

We interpret the high tension inside a computer like a "1", and the low tension like a "0".

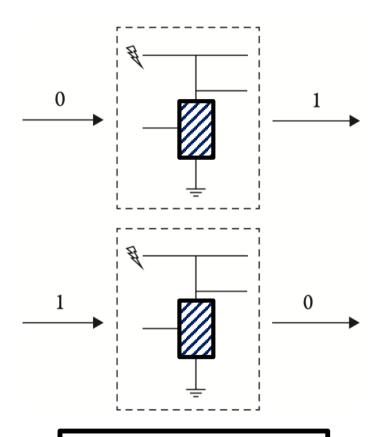This is an encoding: it maps two entities in the real world onto a set of natural numbers (0 and 1).




With such encoding in mind, a single transistor acts like a system which replies with "1" when we give it "0", and viceversa.



We will use this graphical organization of multiple cases. Case 1 is when we give the system "0" in input and obtain "1" in output.

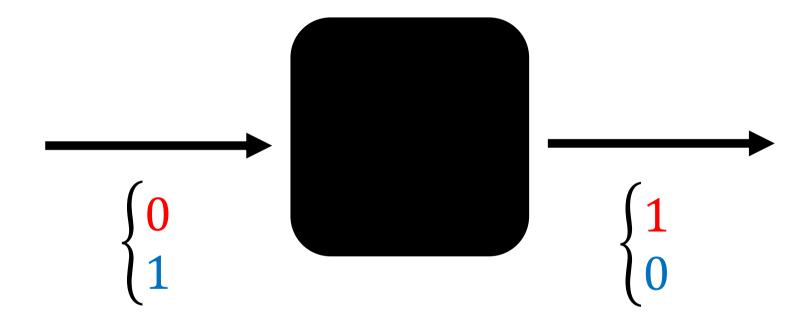Case 2 is when we give "1" in input and obtain "0" in output.



What to do with a system with this behavior?

 $\mathbf{v}_{_{\mathbf{a}}}$  ----- 1 ----- true

If we use '0' to encode the concept of "false", and '1' to encode "true", we are moving from arithmetic with numbers to logic with truth values.


Let's introduce another encoding on top of the fundamental one.

Logic is the discipline that formalizes reasoning, that is, aims at making reasoning (e.g. "all men are mortal; Socrates is a man; hence, Socrates is mortal") rigorous by transforming sentences in sequences of symbols (called formulas) that are manipulated by means of rules.

"False" and "true" are "truth values" that we assign to formulas. Logic does not help us establish the truth values of hypotheses from the real world (e.g. "does God exist?") but it supports us in checking whether a certain way of reasoning is correct or not.



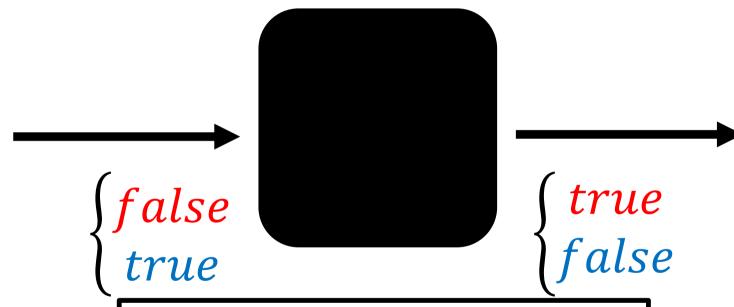
Let's take a look at the system again, with the logic-oriented encoding in mind.




When we give it "false", it replies with "true". When we give it "true", it replies with "false".


The system acts like a "not". Indeed, "not false" is the same as "true", and "not true" is the same as "false".

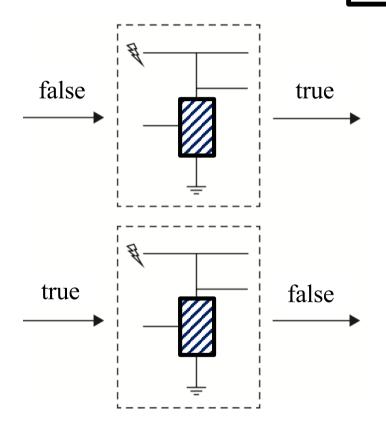A transistor can then be seen as the electronic embodiment of the "negation" operator in logic.



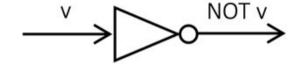

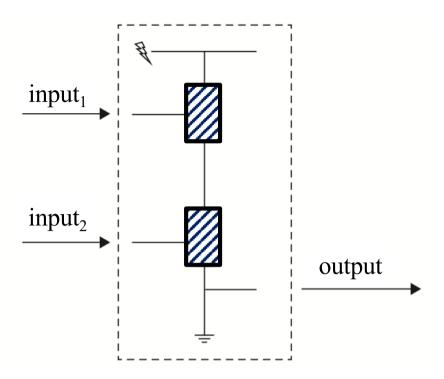This is how a system that negates, also known as "NOT gate" ("gate" because the electric signal goes through it), is represented in the graphical standard for circuit design.




Let's build more complex systems, by using more than one transistor. This system has two inputs and one output.

The transistors are said to be in a "serial" configuration, because they are one after the other (i.e. in a series) between the high tension and the ground.

The tension in the output point is high only when the point is directly connected to the high tension above. This means that both transistors must be conductive, which means that both inputs must be high.

In numerical terms, since we have 2 inputs, we have 4 cases  $(4 = 2^2)$ , and the output is 1 only in one case  $(input_1 = 1 \text{ and } input_2 = 1)$ 

input₁	input <sub>2</sub>	output
0	0	0
0	1	0
1	0	0
1	1	1

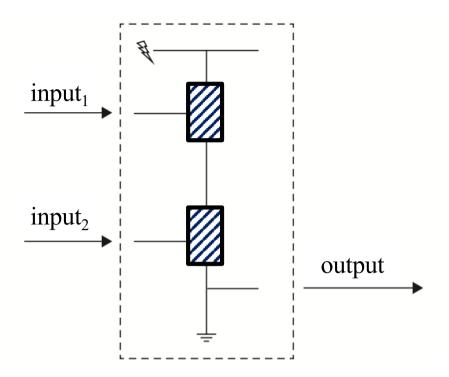



In logical terms, the output is "true" only when both inputs are "false". In other words, just one false input is enough to make the output false.

input₁	input <sub>2</sub>	output
false	false	false
false	true	false
true	false	false
true	true	true

The two inputs are put together in the same way we use the "AND" conjunction: "the Sun is cold AND one plus one is two" is false, whereas "water is a liquid AND seven is an odd number" is true. This circuit may be seen as the electronic version of the AND logical operator.

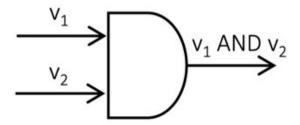This is how an "AND gate" is represented in the graphical standard for circuit design.



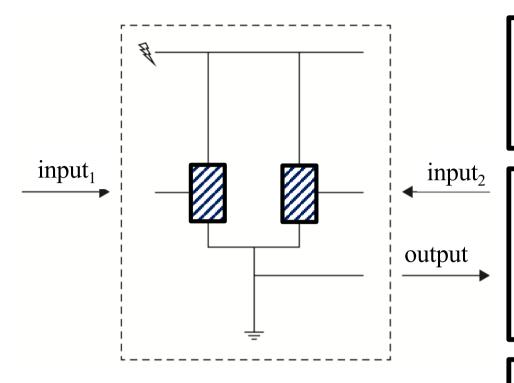


In this other system, the two transistors are said to be in a "parallel" configuration, because they are one next to the other (i.e. on parallel lines) between the high tension and the ground.

The tension in the output point is high in more cases here, because for the output point to be connected to the high tension we just need one transistor to be condictive. This means that only when both transistors are off the output is low tension.

In numerical terms, the output is 0 only in one case (input<sub>1</sub> = 0 and input<sub>2</sub> = 0)

input₁	input <sub>2</sub>	output
0	0	0
0	1	1
1	0	1
1	1	1

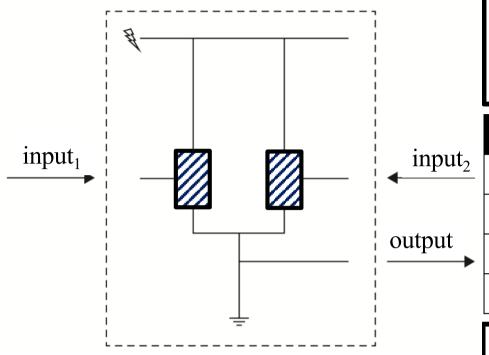

In logical terms, the output is "false" only when both inputs are "false" and "true" in all other cases. We need one true input to make the output true as well.

input₁	input <sub>2</sub>	output
false	false	false
false	true	true
true	false	true
true	true	true

The two inputs are put together in the same way we use the "OR" conjunction (also known as "disjunction"): "the Sun is cold OR one plus one is three" is false, whereas "water is a liquid OR the Earth if flat" is true.

This circuit may be seen as the electronic version of the OR logical operator.

This is how an "OR gate" is represented in the graphical standard for circuit design.

